

Duration

50 minutes

Submit your answers in the order of questions

2 points penalty for wrong order

Wrong/No Roll Number or Name

Zero points for the Quiz

Wrong/No Instructor Name

2 points will be deducted from the total

Roll Number	EE18B122
Name	AKILESH KANNAN
Instructor's Name	Prof - Ananth Krishnan

For Office Use only [1] :-

Question:	1	2	3	Total
Points:	6	3	3	12
Score:				

This exam has 3 questions, for a total of 12 points.

1. (6 points) Design a minimal gate level implementation and draw a minimal gate level circuit diagram for finding the square of a given positive decimal number N , with following conditions

- Input to the circuit is the unsigned binary form of decimal number N
- N is represented in binary by 2.1 bits as $(N)_{10} = (ab.c)_2$ where a, b , and c are bits. So, N is represented by 2 bits (a and b) for integer part and 1 bit (c) for fractional part. For example, if $ab.c = 10.1$, so, $a = 1, b = 0$ and $c = 1$, then, $(N)_{10}$ will correspond to the decimal equivalent of $(ab.c)_2$. Hence, a, b , and c will be the inputs to the circuit.
- $(0.0)_{10} \leq (N)_{10} \leq (3.0)_{10}$ or simply $(0.0 \leq N \leq 3.0)$
- the output of the circuit should be the Binary equivalent of $(N^2)_{10}$ {For

example, if, $(N)_{10} = (2.0)_{10}$, then, the output should be binary form of $(N^2)_{10}$. In this case, the output would be binary form of $(4.00)_{10}$.


- The binary output should be represented by sufficient number of bits for Accurately representing, both the integer and fractional parts.
 - only AND, OR and NOT gates are to be used.
2. (3 points) Draw the minimal NOR gate based implementation of the following function.
- $$F(A, B, C, D) = \sum m(0, 3, 5, 7, 8, 9, 10, 12, 13) + \sum d(1, 6, 11, 14)$$
3. (3 points) A majority circuit is a combinational circuit, whose output is equal to 1, when the input variables have more 1s than 0s. The output is zero otherwise. Design a three-input majority function using 4 : 1 MUX.

TRUTH TABLE for the squaring operation

INPUTS			INTEGRAL			FRACTIONAL		
a	b	c	w	x	z	y	q	r
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	0	0	1	0	0
Don't	Don't	Don't	X	X	X	X	X	X

Given number is < 3.0 (11.0).

So, overflow is
DON'T CARE CASE

 

Taking 4 digits for integral & 2 bits for

fractional. as max integer bits = 4 (for $2^4 = 16$)

Max frac. bits for $(0.1)^2 = (0.01)$

Multiplier for x

a	b	00	01	11	10
0	0	m0	m1	m2	m3
1	0	m4	m5	m6	m7

$$x = ab$$

Reduction for g

		b			
		00	01	11	10
a	0	m_0	m_1	m_3	m_4
	1	m_2	m_5	m_7	m_6

c

m_4, m_5, m_6, m_7

$$= ab'$$

Reduction for z

		b			
		00	01	11	10
a	0	m_0	m_1	m_3	m_4
	1	m_2	m_5	m_7	m_6

c

$$z = ac + bc$$

$$= (a+b)c$$

Reduction for w

		b			
		00	01	11	10
a	0	m_0	m_1	m_3	m_4
	1	m_2	m_5	m_7	m_6

c

$$w = bc'$$

for P

$$P = 0$$

for all n/p


for q :

		b			
		00	01	11	10
a	0	m_0	m_1	m_3	m_4
	1	m_2	m_5	m_7	m_6

c

$$\boxed{1q = c}$$

 
\Rightarrow the circuit implementation is.



Expressions : $xyzw, pq$


$$(abc)^2 = (xyzwpq)^2$$
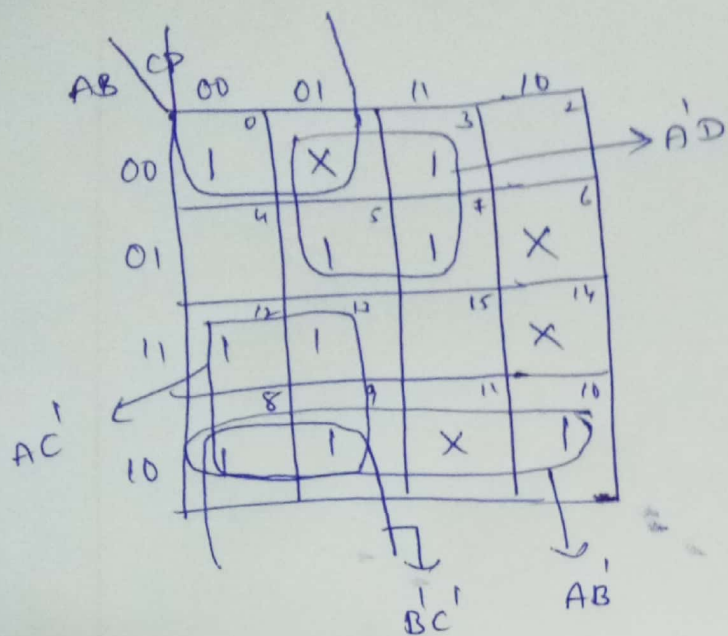
$$\begin{aligned} x &= ab \\ y &= ab' \\ z &= (a+b)c \\ w &= bc' \\ p &= d \\ q &= c \end{aligned}$$





K-MAP - 1 MARK
 EXPRESSION - 1 MARK
 CIRCUIT/DIAGRAM - 1 MARK

$$F = AC' + BC' + AB + A'D$$

 

[α]

  

$$F = (A+C'+D)(A+B'+D)(A'+B'+C')$$


→ Let the 3 inputs be A, B, C, & Output be Y

Truth table (for the given i/p, o/p map)

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

K-Map

(2)

 

→ Identifying the truth table / K-Map - (1 mark)

Realization with 4:1 Mux - (2 marks)

