

## EE2001-Tutorial 6


Date: 6<sup>th</sup> March 2018

More on Synchronous Sequential Logic including Register

TAs : Sreeraj S J (Qns – 1, 3, 5, 7, 9) & Ragul S (Qns – 2, 4, 6, 8, 10)

1) (i) Design a sequential circuit with two D flip-flops A and B, and one input  $x_{in}$ . When  $x_{in} = 0$ , the state of the circuit remains the same. When  $x_{in} = 1$ , the circuit goes through the state transitions from 00 to 01, to 11, to 10, back to 00, and repeats.

Ans 1(i) state Diagram.

 

$A(t+1)$


$x \backslash AB$	00	01	11	10
0			1	1
1		1	1	

$$A(t+1) = \bar{x}A + xB$$

$B(t+1)$


$x \backslash AB$	00	01	11	10
0		1	1	
1	1	1		

$$B(t+1) = \bar{x}B + x\bar{A}$$

 

(ii) Design a one-input, one-output serial 2's complementer. The circuit accepts a string of bits from the input and generates the 2's complement at the output. The circuit can be reset asynchronously to start and end the operation.

(ii)

 

Rule used  
 → Untill first '1', continue the bits; after that - reverse the bits

	$A(t+1)$	
	0	1
$x$		
0	0	1
1	1	1


$$A(t+1) = A + x$$

	$y$	
	0	1
$x$		
0	0	1
1	1	0

$$y = A\bar{x} + \bar{A}x$$

$$= A \oplus x$$

Circuit:

 

2) Design a sequential circuit with two JK flip-flops A and B and two inputs E and F. If  $E = 0$ , the circuit remains in the same state regardless of the value of F. When  $E = 1$  and  $F = 1$ , the circuit goes through the state transitions from 00 to 01, to 10, to 11, back to 00, and repeats. When  $E = 1$  and  $F = 0$ , the circuit goes through the state transitions from 00 to 11, to 10, to 01, back to 00, and repeats.

State Table:

Present state		Inputs		Next state		Flip-flop inputs			
A	B	E	F	A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

JK Flip-flop:

$Q_n$	J	K	$Q_{n+1}$
0	0	X	0
0	1	X	1
1	X	1	0
1	X	0	1

EF \ AB	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

$$J_A = E (BF + B'F')$$

EF \ AB	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	0	1	0
10	0	0	0	1

$$k_A = E (BF + B'F')$$


EF \ AB	00	01	11	10
00	0	0	1	1
01	X	X	X	X
11	X	X	X	X
10	0	0	1	1

$$J_B = E$$


EF \ AB	00	01	11	10
00	X	X	X	X
01	0	0	1	1
11	0	0	1	1
10	X	X	X	X

$$k_B = E$$

Circuit Diagram:

 

 3) A sequential circuit has three flip-flops A, B, C ; one input  $x_{in}$ ; and one output  $y_{out}$ . The state diagram is shown. The circuit is to be designed by treating the unused states as don't-care conditions. Analyze the circuit obtained from the design to determine the effect of the unused states. (a) Use D flip-flops in the design. (b) Use JK flipflops in the design.



3.

	Present state			input $x$	Next state			output $y$
	A	B	C		A	B	C	
0	0	0	0	0	0	1	1	0
1	0	0	0	1	1	0	0	1
2	0	0	1	0	0	0	1	0
3	0	0	1	1	1	0	0	1
4	0	1	0	0	0	1	0	0
5	0	1	0	1	0	0	0	1
6	0	1	1	0	0	0	1	0
7	0	1	1	1	0	1	0	1
8	1	0	0	0	0	1	0	0
9	1	0	0	1	0	1	1	0

Unused  $\Rightarrow$  Don't care

$$d(A, B, C, x) = \sum (10, 11, 12, 13, 14, 15)$$

(i) Using D-Flip-flops:

$$D_A = \bar{A} \bar{B} x$$

$$D_B = A + \bar{C} \bar{x} + BCx$$

$$D_C = Ax + C\bar{x} + \bar{A} \bar{B} \bar{x}$$

$$y = \bar{A} x$$

Unused State table.

Present State			Input	Next State			Output
A	B	C	x	A	B	C	y
1	0	1	0	0	1	1	0
1	0	1	1	0	1	1	0
1	1	0	0	0	1	0	0
1	1	0	1	0	1	1	0
1	1	1	0	0	1	1	0
1	1	1	1	0	1	1	0

For All unused states transit to Used states (011, 010).

So circuit is self correcting.

(ii) With J-K flip flops

$$J_A = \bar{B}x$$

$$J_B = A + \bar{C}x$$

$$J_C = Ax + \bar{A}\bar{B}x$$

$$K_A = 1$$

$$K_B = \bar{C}x + C\bar{x}$$

$$K_C = x.$$


$$y = \bar{A}x.$$

Q(t)	Q(t+1)	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Here  $K_A = 1$ ; which sets  $Q_A = 0$


The circuit is self correcting.

 4) Develop the state diagram for a state machine that detects a sequence of three or more consecutive 1's in a string of bits coming through an input line.



5) Include a 2-input NAND gate in the given register shown and connect the gate output to the C inputs of all the flip-flops. One input of the NAND gate receives the clock pulses from the clock generator, and the other input of the NAND gate provides a parallel load control. Explain the operation of the modified register. Explain why this circuit might have operational problems.

5.

 


When  $LOAD = 0$  ;  
output is HIGH ; irrespective of  
CLOCK signal.  
when  $LOAD = 1$   
output is  $\overline{CLOCK}$



Since the flip flops are Edge triggered, the  
HIGH logic at C doesn't matter.

Possible Operational Problems:

 - (1). The additional delay introduced by the gated clock affects the synchronicity of this register with other elements which are working in tandem.



  6) Include a synchronous clear input to the given register. The modified register will have a parallel load capability and a synchronous clear capability. The register is cleared synchronously when the clock goes through a positive transition and the clear input is equal to 1.





7) (i) What is the difference between serial and parallel transfer? Explain how to convert serial data to parallel and parallel data to serial. What type of register is needed?

(ii) The contents of a four-bit register is initially 0110. The register is shifted six times to the right with the serial input being 1011100. What is the content of the register after each shift?

7 (i) Serial transfer :

→ Transfers 1 bit data with the clock

→ To transfer  $N$  bits ;  $[N \times \text{Clock Period}]$  time is taken.


Parallel transfer.

→ Transfers multiple bits with clock

→ To transfer  $N$  bits ;  $\left[ \frac{N \times \text{Clock Period}}{K} \right]$  time is taken ;  $\left\{ K \Rightarrow \text{No. of parallel lines} \right\}$

SERIAL - IN PARALLEL OUT

4-bit Example.

 


## PARALLEL IN SERIAL OUT

(4-bit example)

Set  $\overline{LOAD} = 0$  to load the parallel data

 Set  $\overline{SHIFT/LOAD} = 1$  to transfer data serially.



D-type flip-flops are used to make these registers


(ii)

	A	B	C	D
Initial stage :	0	1	1	0
1 <sup>st</sup> pulse :	1	0	1	1
2 <sup>nd</sup> pulse :	0	1	0	1
3 <sup>rd</sup> pulse :	1	0	1	0
4 <sup>th</sup> pulse :	1	1	0	1
5 <sup>th</sup> pulse :	1	1	1	0
6 <sup>th</sup> pulse :	0	1	1	1


8) The given four-bit universal shift register is enclosed within one IC component package.

(a) Draw a block diagram of the IC showing all inputs and outputs. Include two pins for the power supply.

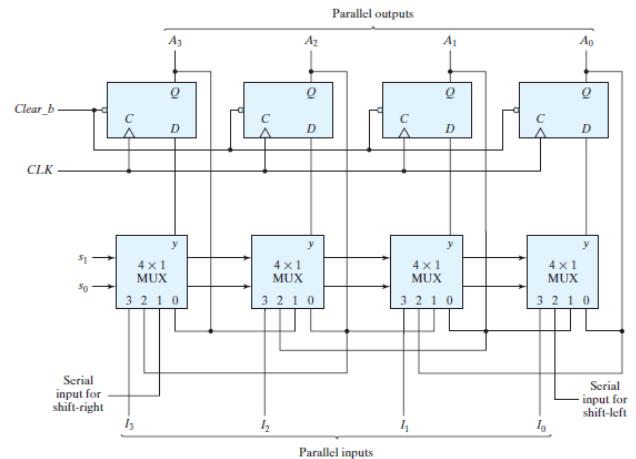(b) Draw a block diagram using two of these ICs to produce an eight-bit universal shift register.




**Block diagram:**

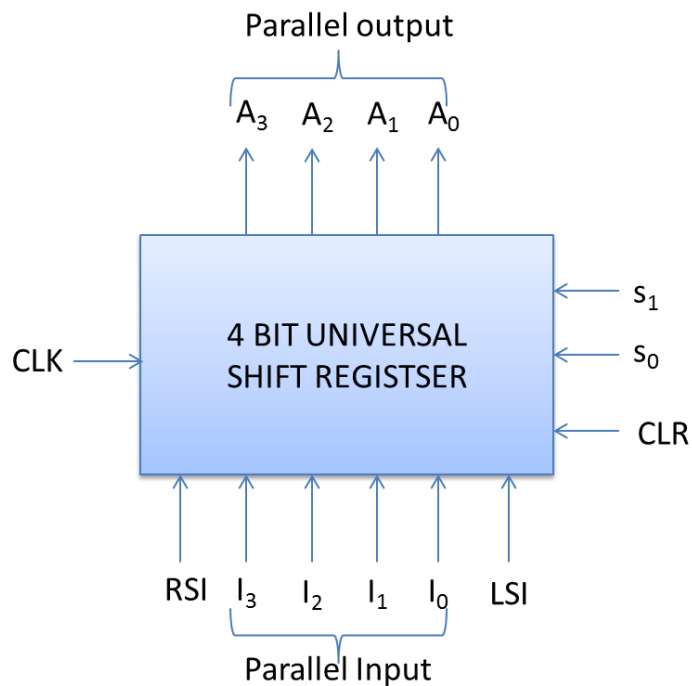


S1	S0	Register operation
0	0	No change
0	1	Shift right with RSI
1	0	Shift left with LSI
1	1	Parallel load

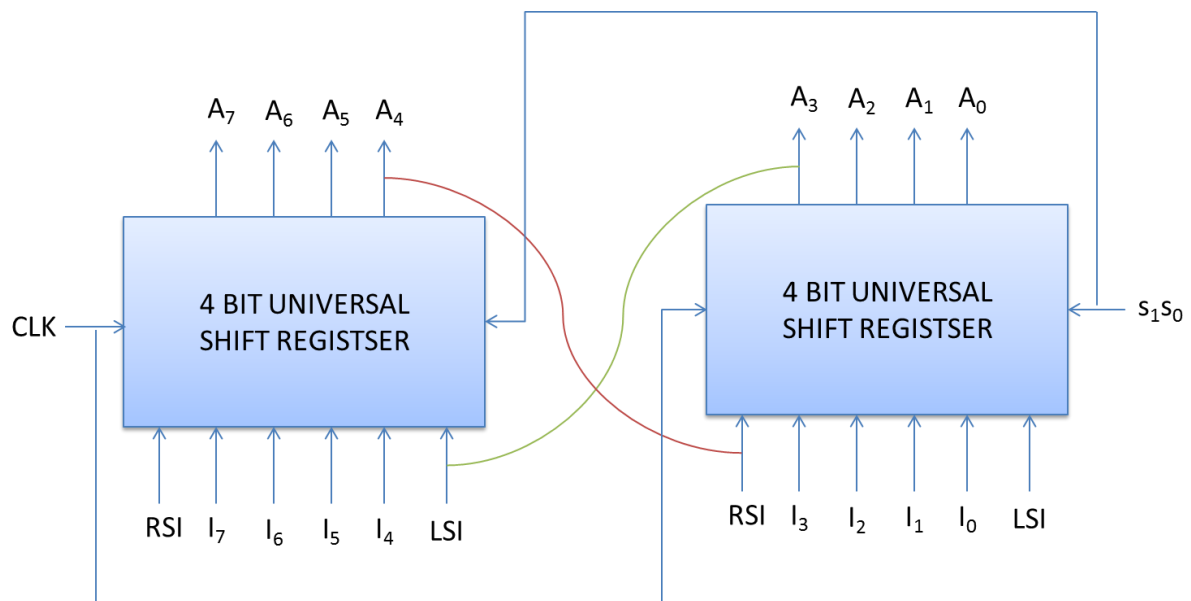**8-bit universal shift register using two 4-bit shift registers:**



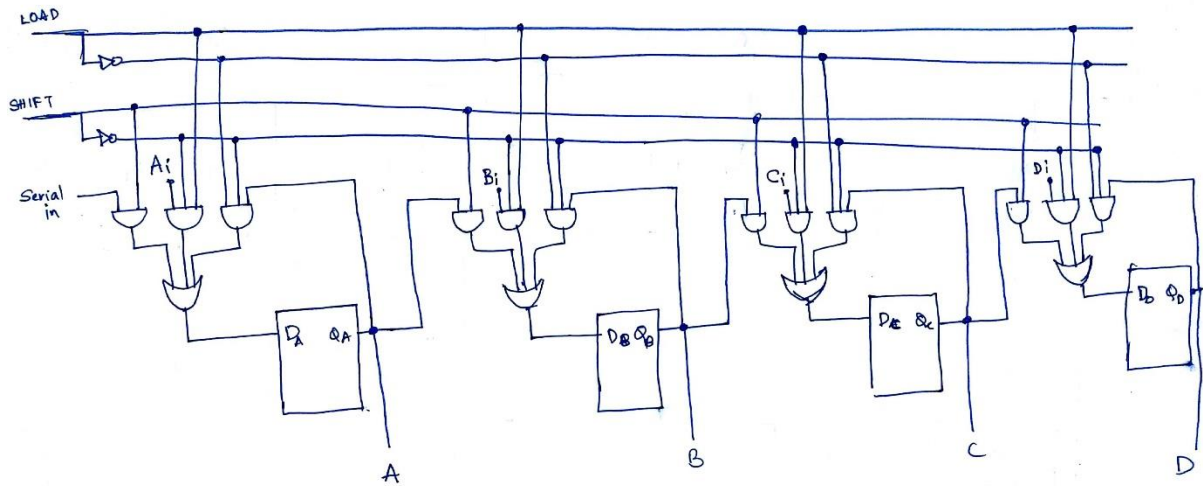
9) (i) Design a four-bit shift register with parallel load using D flip-flops. There are two control inputs: shift and load. When shift = 1, the content of the register is shifted by one position. New data are transferred into the register when load = 1 and shift = 0. If both control inputs are equal to 0, the content of the register does not change.




(when  $SHIFT = 1$ , irrespective of  $LOAD$  bit, System will operate in Serial shift mode)

(ii) Draw the logic diagram of a four-bit register with four D flip-flops and four  $4 \times 1$  multiplexers with mode selection inputs  $s_1$  and  $s_0$ . The register operates according to the following function table.

$s_1$	$s_0$	Register Operation
0	0	No change
1	0	Complement the four outputs
0	1	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data

 

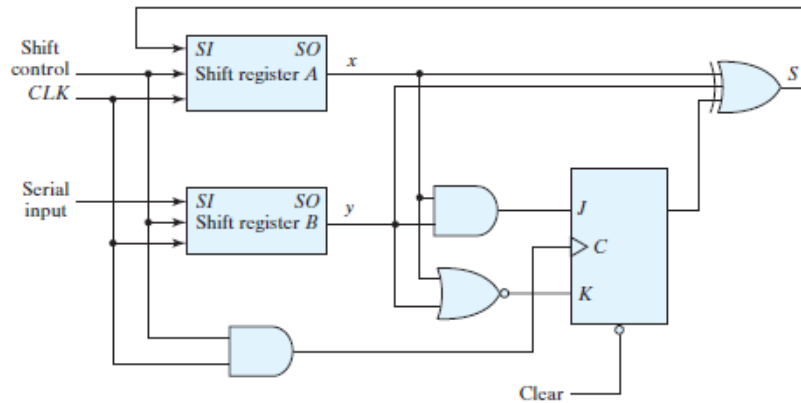10) The given serial adder uses two four-bit registers. Register A holds the binary number 0101 and register B holds 0111. The carry flip-flop is initially reset to 0. List the binary values in register A and the carry flip-flop after each shift.



Shift Register A				Shift Register B				JK flip-flop				S
A3	A2	A1	A0	B3	B2	B1	B0	Q <sub>n</sub>	J	K	Q <sub>n+1</sub>	
0	1	0	1	0	1	1	1	0	1	0	1	0
0	0	1	0	-	0	1	1	1	0	0	1	0
0	0	0	1	-	-	0	1	1	1	0	1	1
1	0	0	0	-	-	-	0	1	0	1	0	1
1	1	0	0									

**Verification:**

$A + B = 0101 + 0111 = 1100$ (A value) with 0 carry (flip-flop output)