 


EE2001: Tutorial 3 Solutions

TA: Arnab Goswami (Q1-Q5)

Bhargav Somepalli (Q6-Q10)


1. (i)



As the gate and drain terminals of the Q_1 transistor are shorted, it acts as resistor. MOS transistor is bilateral. So we have two similar paths AED and CEB (other than AB and CD), that connect the output to ground.


Output $Y = (AB + CD + AED + CEB)'$

(ii)

 

Output $Y = (ABCD)'$

(iii)

 

Output $Y = (A + B + C + D)'$

2. (a) $M = 0$

A	0111
B	0110
<hr/>	
S	01101

$$C = C_4 = 0 \quad C_3 = 1 \quad V = C_4 \oplus C_3 = 1$$

(b) $M = 0$

A	1000
B	1001
<hr/>	
S	10001

$$C = C_4 = 1 \quad C_3 = 0 \quad V = C_4 \oplus C_3 = 1$$

(c) $M = 1$

$$\begin{array}{r}
A \quad \quad 1100 \\
B' \quad \quad 0111 \\
C_0 \quad \quad 1 \\
\hline
\end{array}$$

$$S \quad \quad 10100$$

$$C = C_4 = 1 \quad C_3 = 1 \quad V = C_4 \oplus C_3 = 0$$

(d) $M = 1$

$$\begin{array}{r}
A \quad \quad 0101 \\
B' \quad \quad 0101 \\
C_0 \quad \quad 1 \\
\hline
\end{array}$$

$$S \quad \quad 01011$$

$$C = C_4 = 0 \quad C_3 = 1 \quad V = C_4 \oplus C_3 = 1$$

(e) $M = 1$

$$\begin{array}{r}
A \quad \quad 0000 \\
B' \quad \quad 1110 \\
C_0 \quad \quad 1 \\
\hline
\end{array}$$

$$S \quad \quad 01111$$

$$C = C_4 = 0 \quad C_3 = 0 \quad V = C_4 \oplus C_3 = 0$$

3. Carry lookahead generator consists of two level forms of logic *AND* and *OR*. So this adder is a four level realization. Total delay is:

$$10(XOR) + 5(AND) + 5(OR) + 10(XOR) = 30ns$$

4. (a)

$$\begin{aligned}
(C'_i G'_i + P'_i)' &= (C'_i G'_i)' P_i \\
&= (C_i + G_i) P_i \\
&= C_i P_i + G_i P_i \\
&= C_i (A_i + B_i) + A_i B_i (A_i + B_i) \\
&= C_i A_i + C_i B_i + A_i B_i \\
&= C_{i+1}
\end{aligned}$$

$$\begin{aligned}
(P_i G'_i) \oplus C_i &= (A_i + B_i)(A_i B_i)' \oplus C_i \\
&= (A_i + B_i)(A'_i + B'_i) \oplus C_i \\
&= A_i \oplus B_i \oplus C_i \\
&= S_i
\end{aligned}$$

- (b) Output of *NOR* gate = $(A_o + B_o)' = P'_o$
Output of *NAND* gate = $(A_o B_o)' = G'_o$

$$S_o = (P_o G'_o) \oplus C_o$$

$$C_1 = (C'_o G'_o + P'_o)$$

5. (a)

$$\begin{aligned}
(G_i + P_i C_i)' &= (G_i + P_i)(G_i + C_i)' \\
&= (G'_i P'_i)'(G'_i C'_i)' \\
&= (G'_i P'_i + G'_i C'_i)'
\end{aligned}$$

(b)

$$C_2 = (G'_1 P'_1 + G'_1 C'_1)'$$

$$\begin{aligned}
C_3 &= (G'_2 P'_2 + G'_2 C'_2)' \\
&= (G'_2 P'_2 + G'_2(G'_1 P'_1 + G'_1 C'_1))'
\end{aligned}$$

$$\begin{aligned}
C_4 &= (G'_3 P'_3 + G'_3 C'_3)' \\
&= (G'_3 P'_3 + G'_3(G'_2 P'_2 + G'_2 C'_2))' \\
&= (G'_3 P'_3 + G'_3(G'_2 P'_2 + G'_2(G'_1 P'_1 + G'_1 C'_1)))'
\end{aligned}$$

6. (i) BCD to 9's complement circuit diagram

BCD				9's complement			
A	B	C	D	W	X	Y	Z
0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	0
0	0	1	0	0	1	1	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	0	0
0	1	1	0	0	0	1	1
0	1	1	1	0	0	1	0
1	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0

AB \ CD				
	00	01	11	10
00	1	1	0	0
01	0	0	0	0
11	X	X	X	X
10	0	0	X	X

$$W = A'B'C'$$


AB \ CD				
	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	X	X	X	X
10	0	0	X	X

$$X = B'C + BC' = B \oplus C$$


$$Y = C$$

$$Z = D'$$

Circuit diagram

 

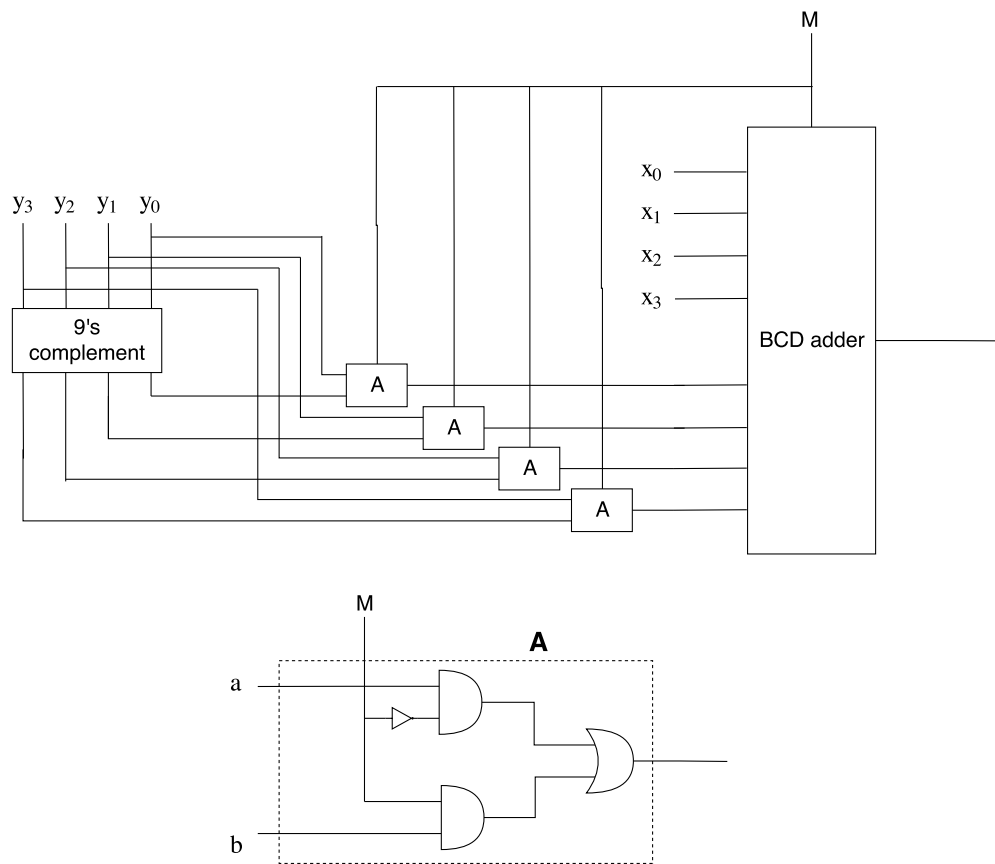- (ii) Consider X, Y to be two BCD numbers.
 $X = x_3x_2x_1x_0$ and $Y = y_3y_2y_1y_0$




M is to select mode.

M = 0 for BCD adder and M = 1 for BCD subtractor.

7. (i) Binary multiplier using AND gates and binary adders

				B_3	B_2	B_1	B_0
				A_3	A_2	A_1	A_0
<hr/>							
				A_0B_3	A_0B_2	A_0B_1	A_0B_0
			A_1B_3	A_1B_2	A_1B_1	A_1B_0	
		A_2B_3	A_2B_2	A_2B_1	A_2B_0		
	A_3B_3	A_3B_2	A_3B_1	A_3B_0			
<hr/>							
P_7	P_6	P_5	P_4	P_3	P_2	P_1	P_0

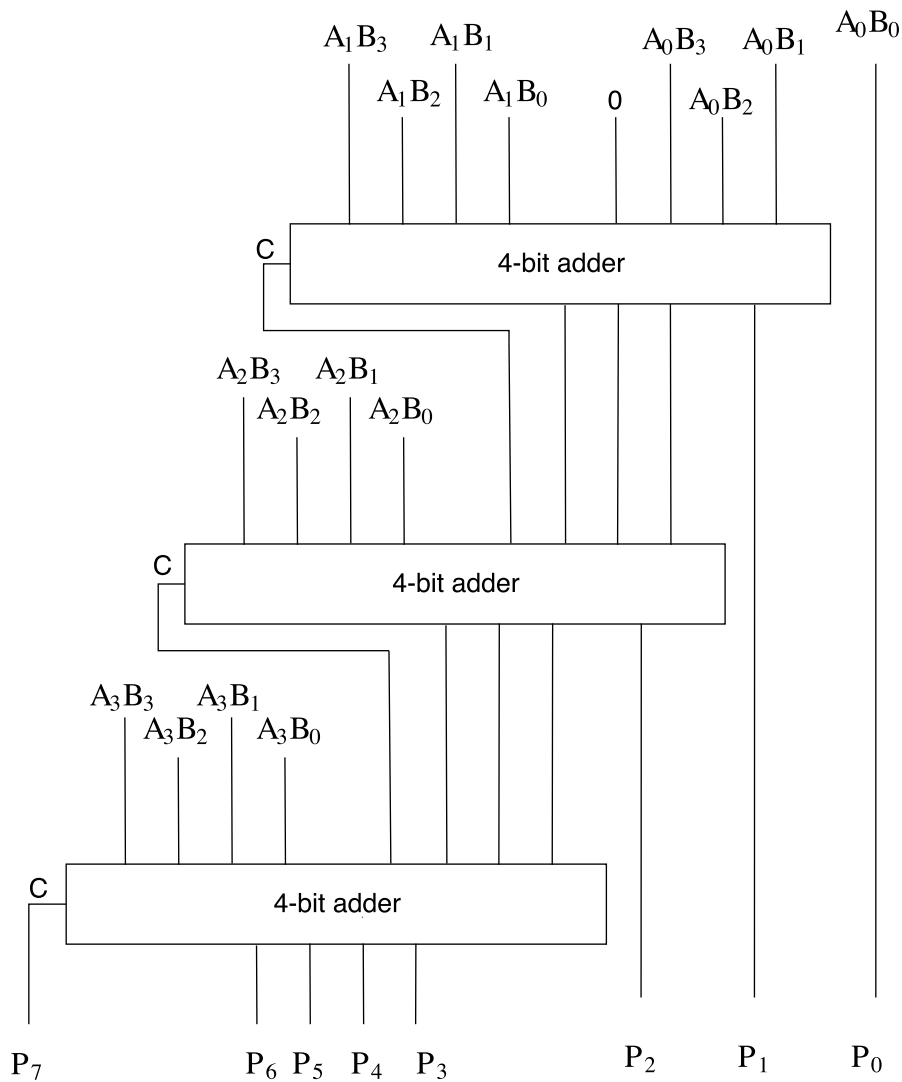


(ii) 4 bit comparator

Consider $A = A_3A_2A_1A_0$ and $B = B_3B_2B_1B_0$

$(A=B) = 1$ if $A_i = B_i$ for all $i = 0, 1, 2, 3$

$= 0$ otherwise

 This can be implemented using XNOR and AND gates.



$$(A=B) = (A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) (A_0 \odot B_0)$$

8. Given $X=x_1x_2x_3x_4$ and $Y=y_1y_2y_3y_4$

- (i) If $G_3 = 1, S_3 = 0$ then $G_4 = 1, S_4 = 0$.
 If $G_3 = 0, S_3 = 1$ then $G_4 = 0, S_4 = 1$.
 If $G_3 = 0, S_3 = 0$, then compare x_4 and y_4 .

G_3	S_3	x_4	y_4	G_4	S_4
0	0	0	0	0	0
0	0	0	1	0	1
0	0	1	0	1	0
0	0	1	1	0	0
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	0
1	1	0	0	X	X
1	1	0	1	X	X
1	1	1	0	X	X
1	1	1	1	X	X

		x_4y_4			
		00	01	11	10
G_3S_3	00	0	0	0	1
	01	0	0	0	0
	11	X	X	X	X
	10	1	1	1	1

$$G_4 = G_3 + S'_3x_4y'_4$$

		x_4y_4			
		00	01	11	10
G_3S_3	00	0	1	0	0
	01	1	1	1	1
	11	X	X	X	X
	10	0	0	0	0

$$S_4 = S_3 + G'_3x'_4y_4$$

(ii) Generalizing the equations,


$$G_i = G_{i-1} + S'_{i-1}x_iy'_i$$

$$S_i = S_{i-1} + G'_{i-1}x'_iy_i$$

$$\therefore G_1 = G_0 + S'_0x_1y'_1 \quad S_1 = S_0 + G'_0x'_1y_1$$

$$G_2 = G_1 + S'_1x_2y'_2 \quad S_2 = S_1 + G'_1x'_2y_2$$

 
$$G_3 = G_2 + S'_2x_3y'_3 \quad S_3 = S_2 + G'_2x'_3y_3$$




9. (i) Binary coded base-seven (BCS)

Decimal	BCS
0	000 000
1	000 001
2	000 010
3	000 011
4	000 100
5	000 101
6	000 110
7	001 000
8	001 001
...	...
...	...

BCS adder using 3-bit binary adders

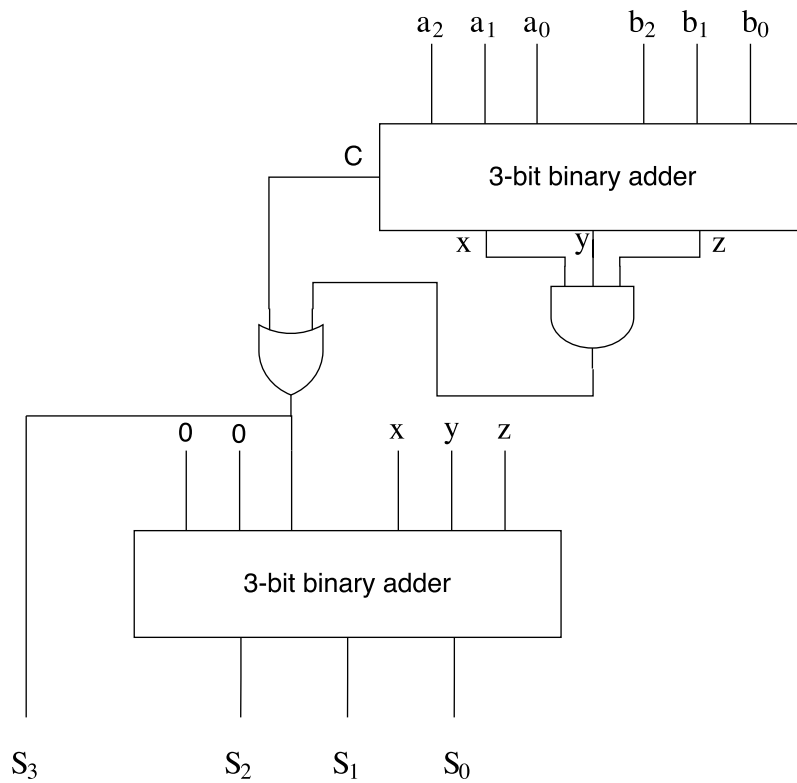

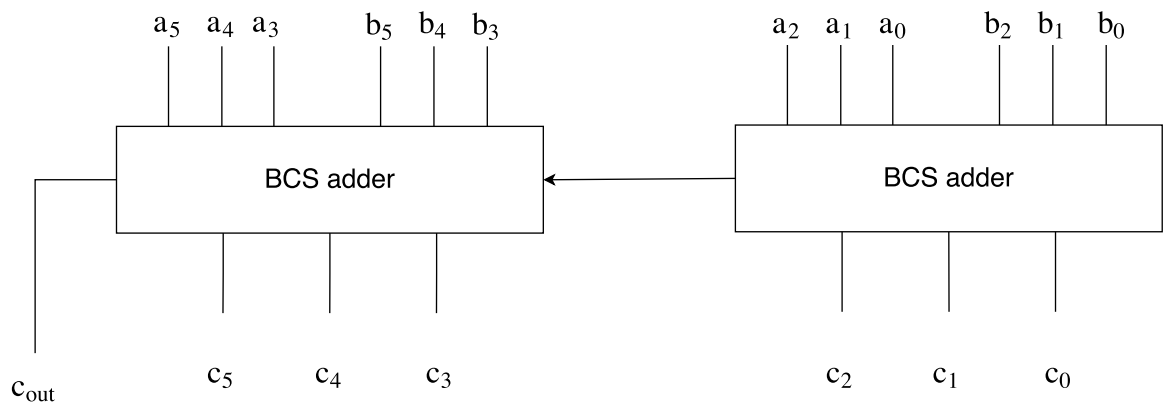(ii) 2-digit BCS adder using two 1-digit BCS adders



10. Seven segment decoder

ABCD	a	b	c	d	e	f	g
0000	1	1	1	1	1	1	0
0001	0	1	1	0	0	0	0
0010	1	1	0	1	1	0	1
0011	1	1	1	1	0	0	1
0100	0	1	1	0	0	1	1
0101	1	0	1	1	0	1	1
0110	1	0	1	1	1	1	1
0111	1	1	1	0	0	0	0
1000	1	1	1	1	1	1	1
1001	1	1	1	1	0	1	1

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	1	1
	11	0	0	0	0
	10	1	1	0	0

$$a = A'C + A'BD + B'C'D' + AB'C'$$

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	1	0	1	0
	11	0	0	0	0
	10	1	1	0	0

$$b = A'B' + A'C'D' + A'CD + B'C'$$

		CD			
		00	01	11	10
AB	00	1	1	1	0
	01	1	1	1	1
	11	0	0	0	0
	10	1	1	0	0

$$c = A'D + A'B + B'C'$$

		CD			
		00	01	11	10
AB	00	1	0	1	1
	01	0	1	0	1
	11	0	0	0	0
	10	1	1	0	0

$$d = A'CD' + A'B'C + B'C'D' + AB'C' + A'BC'D$$

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	0	0	0	1
	11	0	0	0	0
	10	1	0	0	0

$$e = A'CD' + B'C'D'$$

		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	1	1	0	1
	11	0	0	0	0
	10	1	1	0	0

$$f = A'BC' + A'C'D' + A'BD' + AB'C'$$

		CD			
		00	01	11	10
AB	00	0	0	1	1
	01	1	1	0	1
	11	0	0	0	0
	10	1	1	0	0

$$g = A'CD' + A'B'C + A'BC' + AB'C'$$