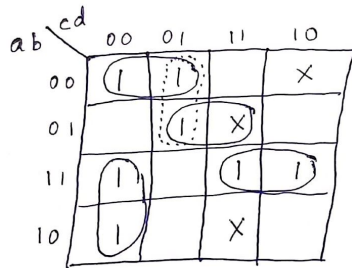


Tutorial 2(In class quiz-solutions)

1. Find the minimum sum-of-products expression for

$$f(a, b, c, d) = \sum m(0, 1, 5, 8, 12, 14, 15) + \sum d(2, 7, 11)$$



$$\Rightarrow a\bar{c}\bar{d} + abc + \bar{a}bd + \bar{a}\bar{b}\bar{c}$$


or

$$a\bar{c}\bar{d} + abc + \bar{a}\bar{c}d + \bar{a}\bar{b}\bar{c}$$

2. Find a minimum sum-of-products and a minimum product-of-sums expression for 'f' and implement using only NOR gates.


$$f(a, b, c, d) = \prod M(0, 2, 10, 11, 12, 14, 15) \cdot \prod D(5, 7)$$

2)

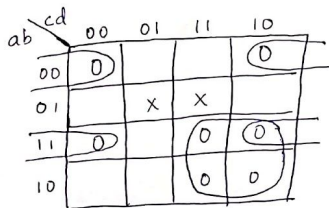

$$\Rightarrow f = (\bar{a} + \bar{c})(\bar{a} + \bar{b} + d)(a + b + d)$$

NOR gate Implementation

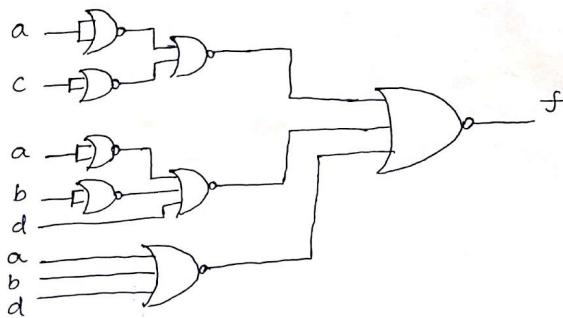


3. find a minimum sum-of-products solution using the Quine-McCluskey procedure.

$$f(a, b, c, d) = \sum m(2, 3, 4, 7, 9, 11, 12, 13, 14) + \sum d(1, 10, 15)$$

sol:

1	0001✓	1, 3	00-1✓	1, 3, 9, 11	-0-1 b'd
2	0010✓	1, 9	-001✓	1, 9, 3, 11	-0-1
4	0100✓	2, 3	001-✓	2, 3, 10, 11	-01- b'c
3	0011✓	2, 10	-010✓	2, 10, 3, 11	-01-
9	1001✓	4, 12	-100 bc'd'	3, 7, 11, 15	--11 cd
10	1010✓	3, 7	0-11✓	3, 11, 7, 15	--11
12	1100✓	3, 11	-011✓	9, 11, 13, 15	1--1 ad
7	0111✓	9, 11	10-1✓	9, 13, 11, 15	1--1
11	1011✓	9, 13	1-01✓	10, 11, 14, 15	1-1- ac
13	1101✓	10, 11	101-✓	10, 14, 11, 15	1-1-
14	1110✓	10, 14	1-10✓	12, 13, 14, 15	11-- ab
15	1111✓	12, 13	110-✓	12, 14, 13, 15	11--
		12, 14	11-0✓		
		7, 15	-111✓		
		11, 15	1-11✓		
		13, 15	11-1✓		
		14, 15	111-✓		

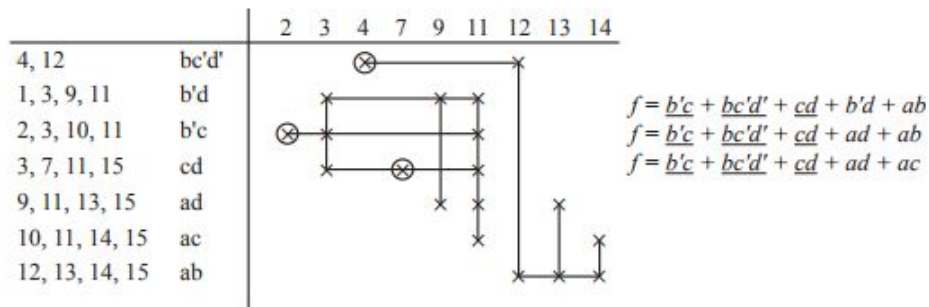Prime implicants: $bc'd'$, $b'd$, $b'c$, cd , ad , ac , ab



Here Essential prime implicants are $b'c$, $bc'd'$, cd

4. Using the method of map-entered variables, use 4-variable maps to find a minimum sum-of-products expression for

$$F(A, B, C, D, E) = \sum m(0, 4, 5, 7, 9) + \sum d(6, 11) + E(m1 + m15),$$

where the m 's represent minterms of the variables A, B, C, D .

sol:

C D \ A B		E = 0			
		00	01	11	10
00		1	1		
01		E	1		1
11			1	E	X
10			X		

$$F = MS_0 + EMS_1 = A'B + A'C'D' + AB'D + E(A'C' + ACD) \text{ or } E(A'C' + BCD)$$

C D \ A B		E = 0			
		00	01	11	10
00		1	1		
01			1		1
11			1		X
10			X		

$$MS_0 = A'C'D' + A'B + A B'D$$

C D \ A B		E = 1			
		00	01	11	10
00		X	X		
01		1	X		X
11			X	1	X
10			X		

$$MS_1 = A'C' + ACD$$

$$MS_1 = A'C' + BCD$$