
 


21/02


DIGITAL SYSTEMSTHURSDAYLATCHES AND FLIP FLOPS

Redrawn as

 

(cross coupled NOR GATES)

S	R	Q(t)	Q*(t+Δ)	P*(t+Δ)	
0	0	0	0	1	} (Check for stability) No change
0	0	1	1	0	
1	0	0	1	0	} → Set condition (Setting Q* to '1')
1	0	1	1	0	
0	1	0	0	1	} → Reset condition (Resets Q* to '0')
0	1	1	0	1	
1	1	0	?	?	} Prohibited condition (Never make S & R 1 at the same instant)
1	1	1	?	?	

 
THIS LATCH IS CALLED AS SET-RESET (SR) LATCH.

⇒ NOT A STABLE STATE


Race - condition

 ⇒ Settles due to difference in delay
 to either $Q \rightarrow 0$ or $Q \rightarrow 1$
 $P \rightarrow 1$ or $P \rightarrow 0$

USING NAND GATES.

 

Active low
set &
Reset.

 

	S	R	Q	Q ⁺	P ⁺
No-change	1	1	0	0	1
	1	1	1	1	0
Set condition	0	1	0	1	0
	0	1	1	1	0
Reset condition	1	0	0	0	1
	1	0	1	0	1
Prohibited condition	0	0	0	?	?
	0	0	1	?	?