
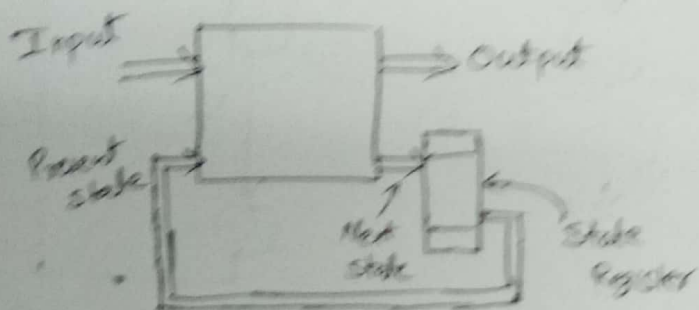



Mealy and Moore Machine

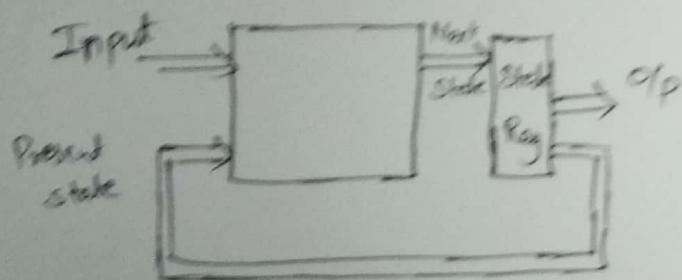


Mealy - O/p is a function of i/p and present state



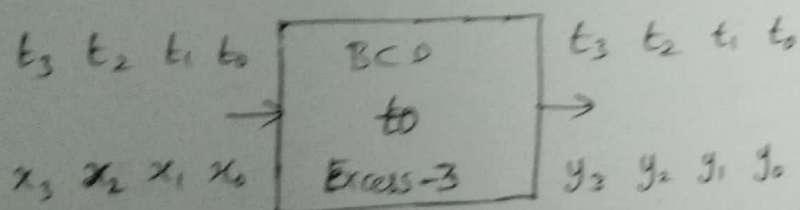Moore - O/p is a function of present state



Serial i/p & Serial o/p

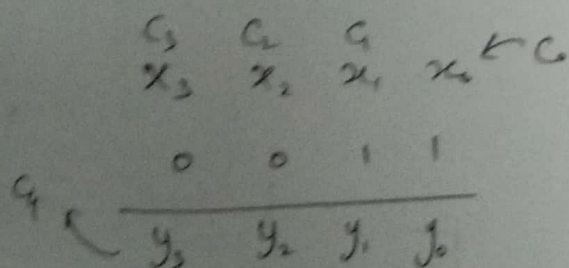

→ We have to remember the carry and at which stage we are in. (In the first & second stage 1 should be added)

S₀

Carry	0	0
x ₀	0	1
bit to be added	1	1
	<u>01</u>	<u>10</u>
(NC)	$\downarrow \downarrow$ c ₁ y ₀	$\downarrow \downarrow$ c ₁ y ₀

(C)

S₁

Carry	0	0
x ₁	0	1
bit to be added	1	1
	<u>01</u>	<u>10</u>
(NC)		(C)

S₂

Carry	1	1
x ₁	0	1
bit to be added	1	1
	<u>100</u>	<u>11</u>
(C)		(C)

S₃

Carry	0	0
x ₂	0	1
bit	0	0
	<u>00</u>	<u>01</u>
(NC)		(NC)

S₄

Carry	1	1
x ₂	0	1
bit	0	0
	<u>01</u>	<u>10</u>
(NC)		(C)

S₅

Carry	0	0
x ₃	0	1
bit	0	0
	<u>00</u>	<u>01</u>
(NC)		(NC)

S₆

Carry	1	1
x ₃	0	1
bit	0	0
	<u>01</u>	<u>10</u>
(NC)		(C)

↓

This never happens when we are converting BCD to Excess-3

